INDIAN INSTITUTE OF TECHNOLOGY

EE-3202

Power System II

Experiment-3

Submitted By:

Shaurya Aggarwal

2301EE56

Fault Analysis

Aim-

Q. The one-line diagram of a simple three-bus power system is shown below. All values are given in per unit (p.u.). Assume a base of 100 MVA and 11 kV.

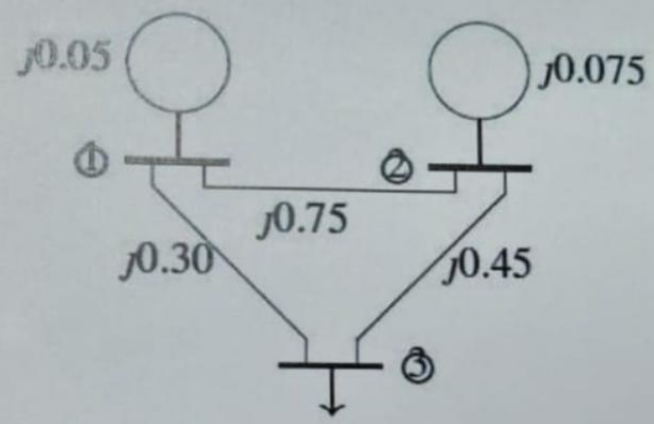

A solid three-phase fault occurs at Bus 3.

- Determine the fault current.
- Determine the voltages at all buses and the line currents during the fault condition.

Verify the obtained results using **MATLAB/Simulink**.
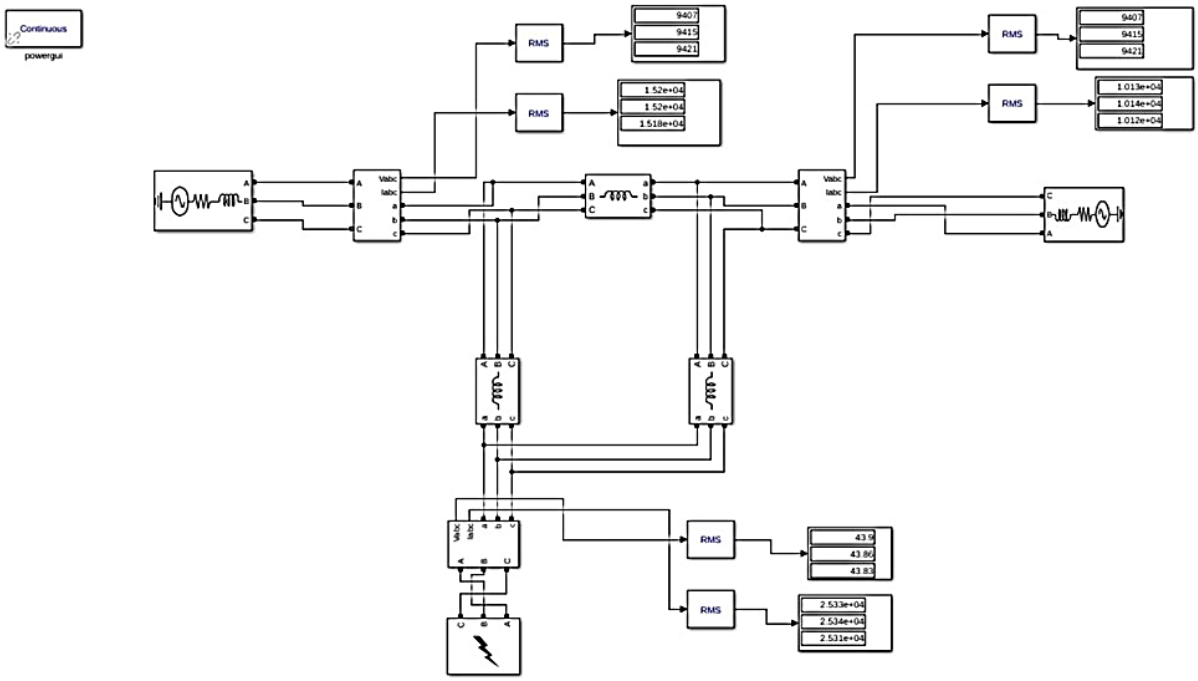
Simulation-